Lab 2 Design Record

Students: Maral Rasuli Arasi, Alaa Khalil, Ruha Javed

RTL Viewer:

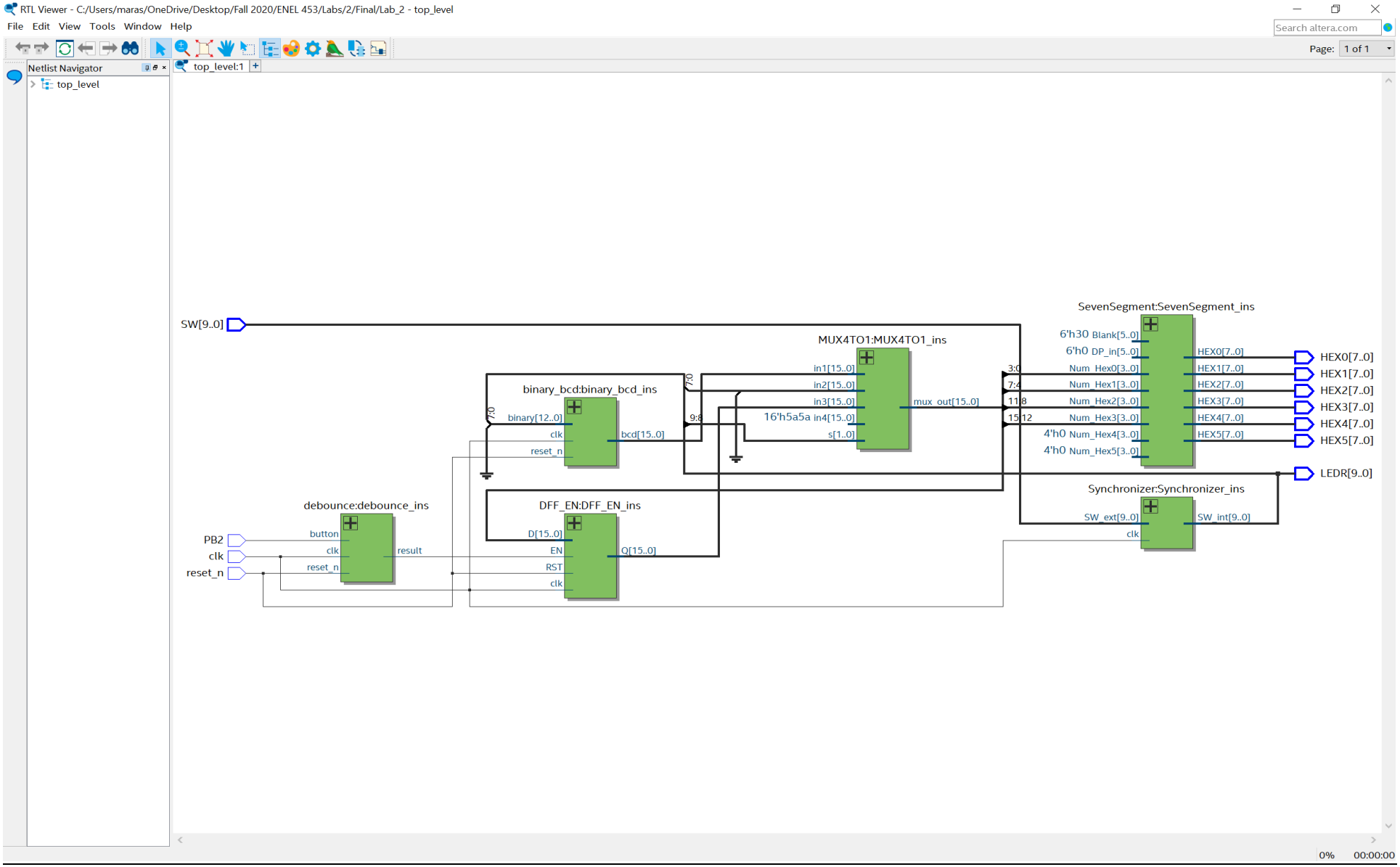

Fmax Summary for 85C Model:

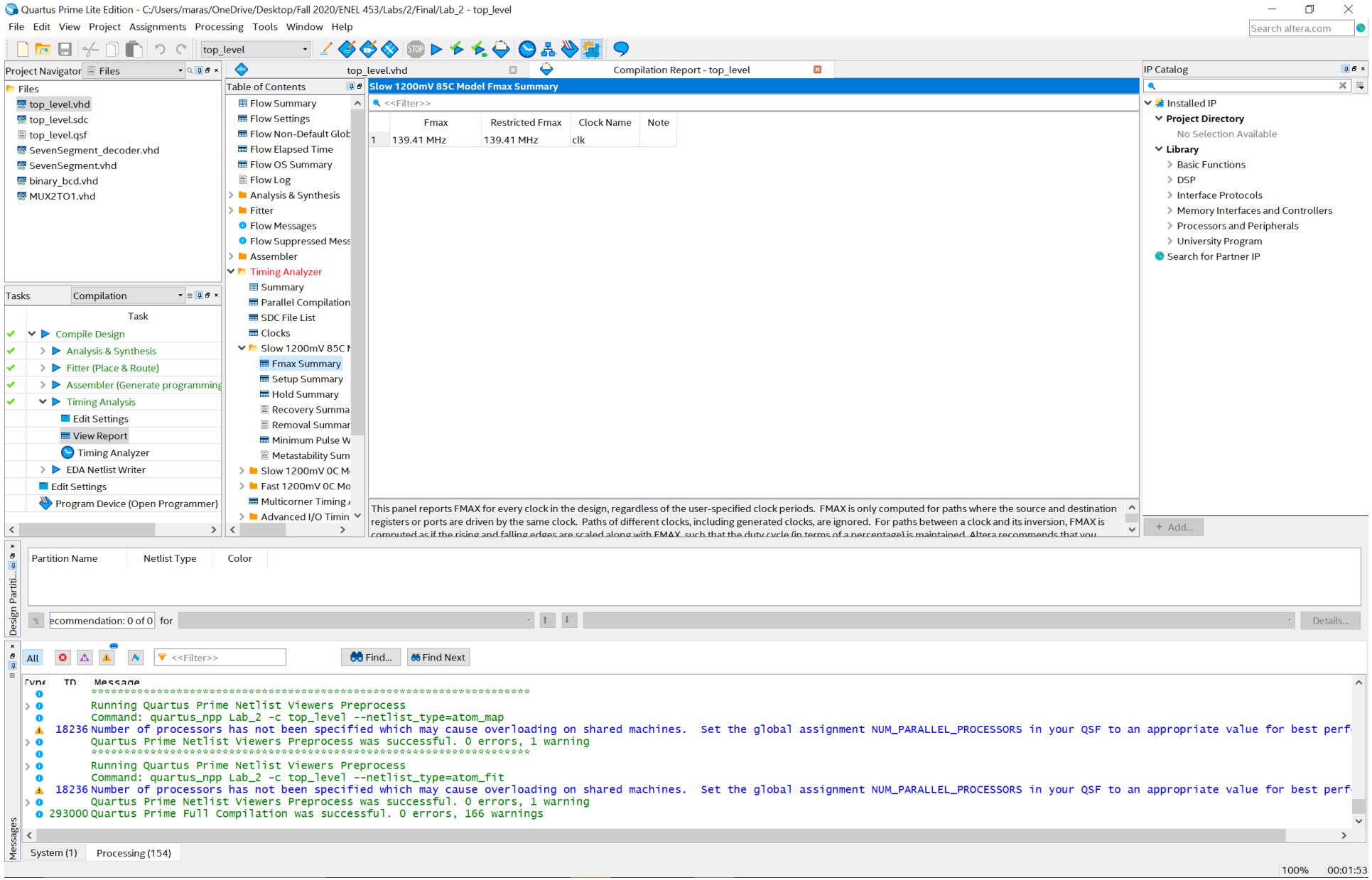

Messages Window:

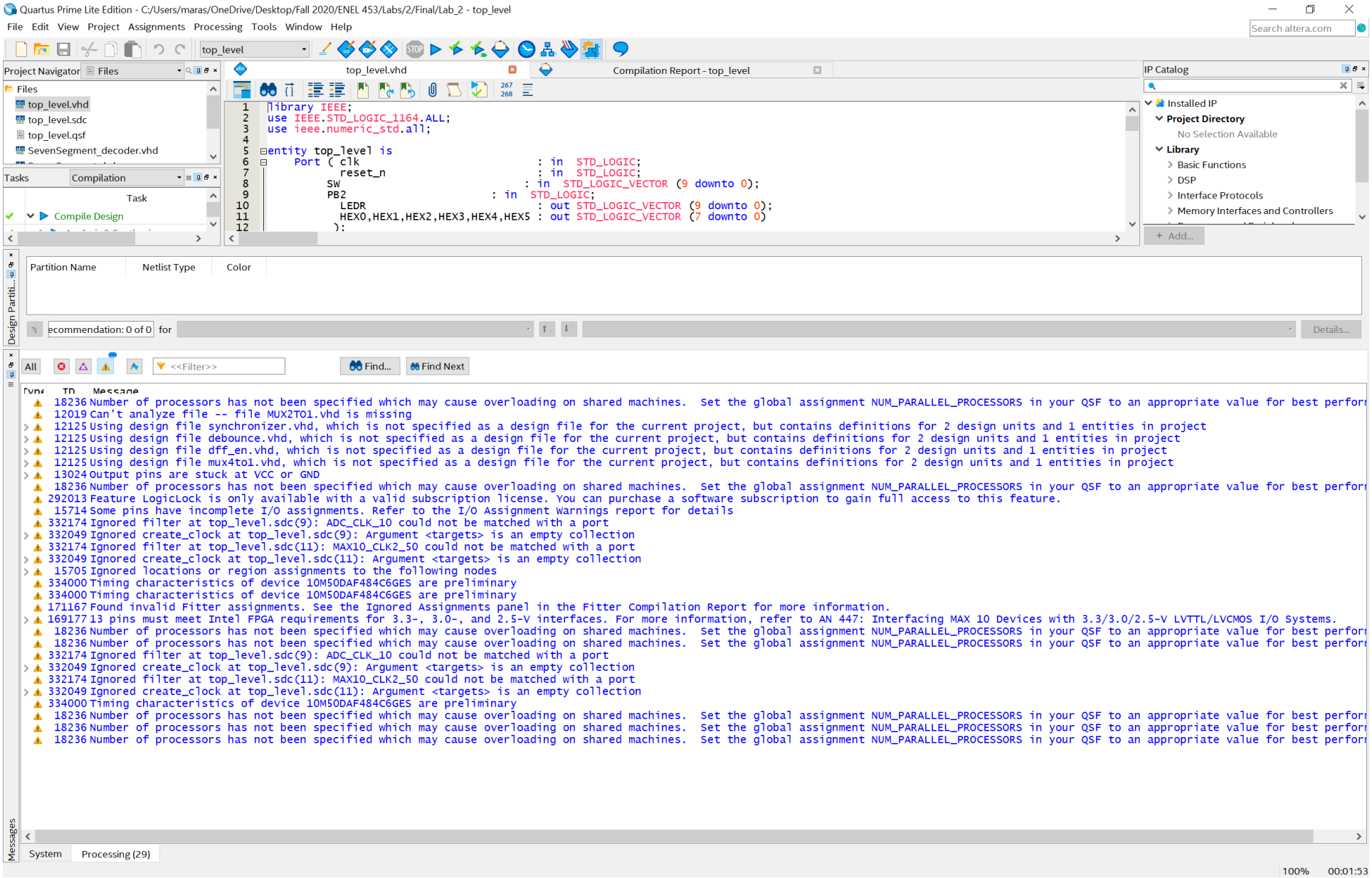

TestBench:

MUX4TO1 Simulation:

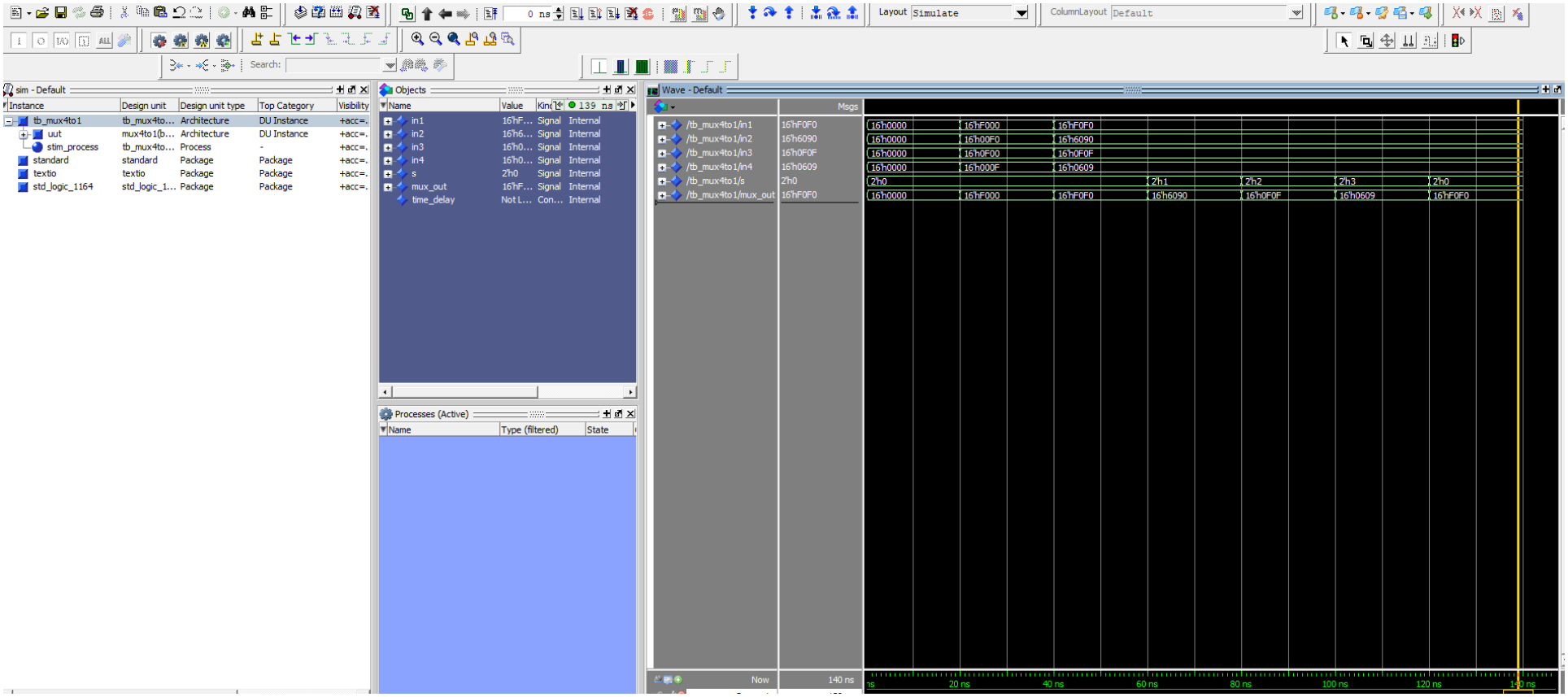

top_level Simulation:

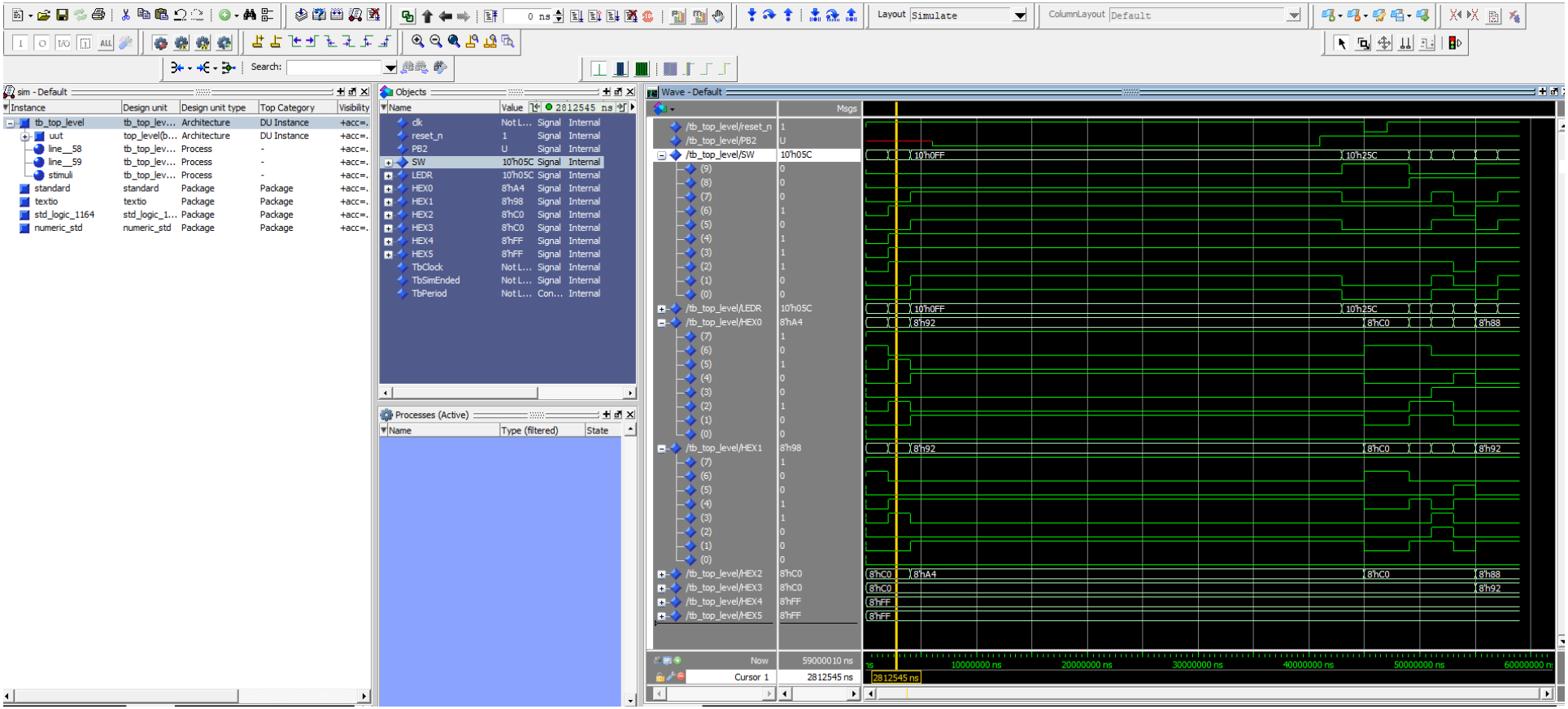

Debounce Simulation:

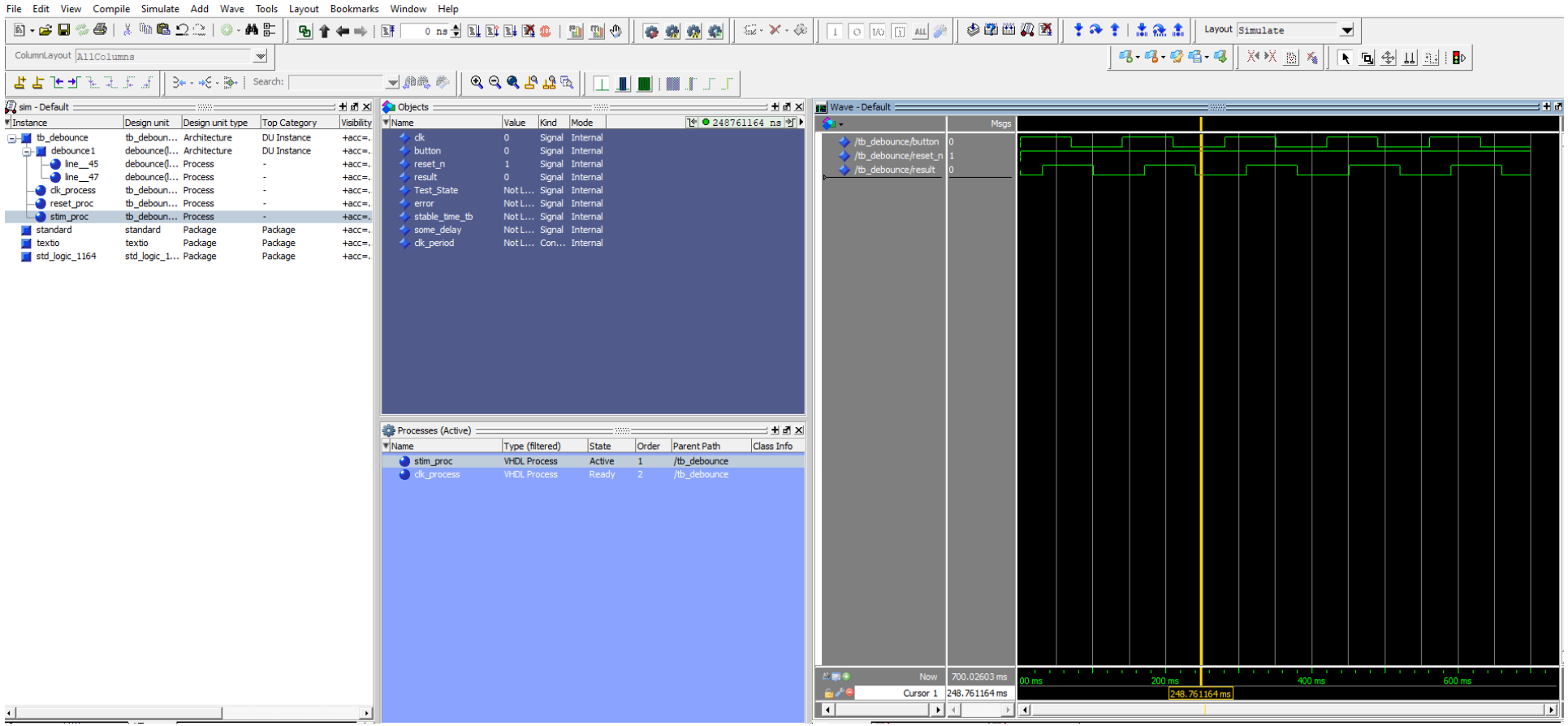

Register Simulation:

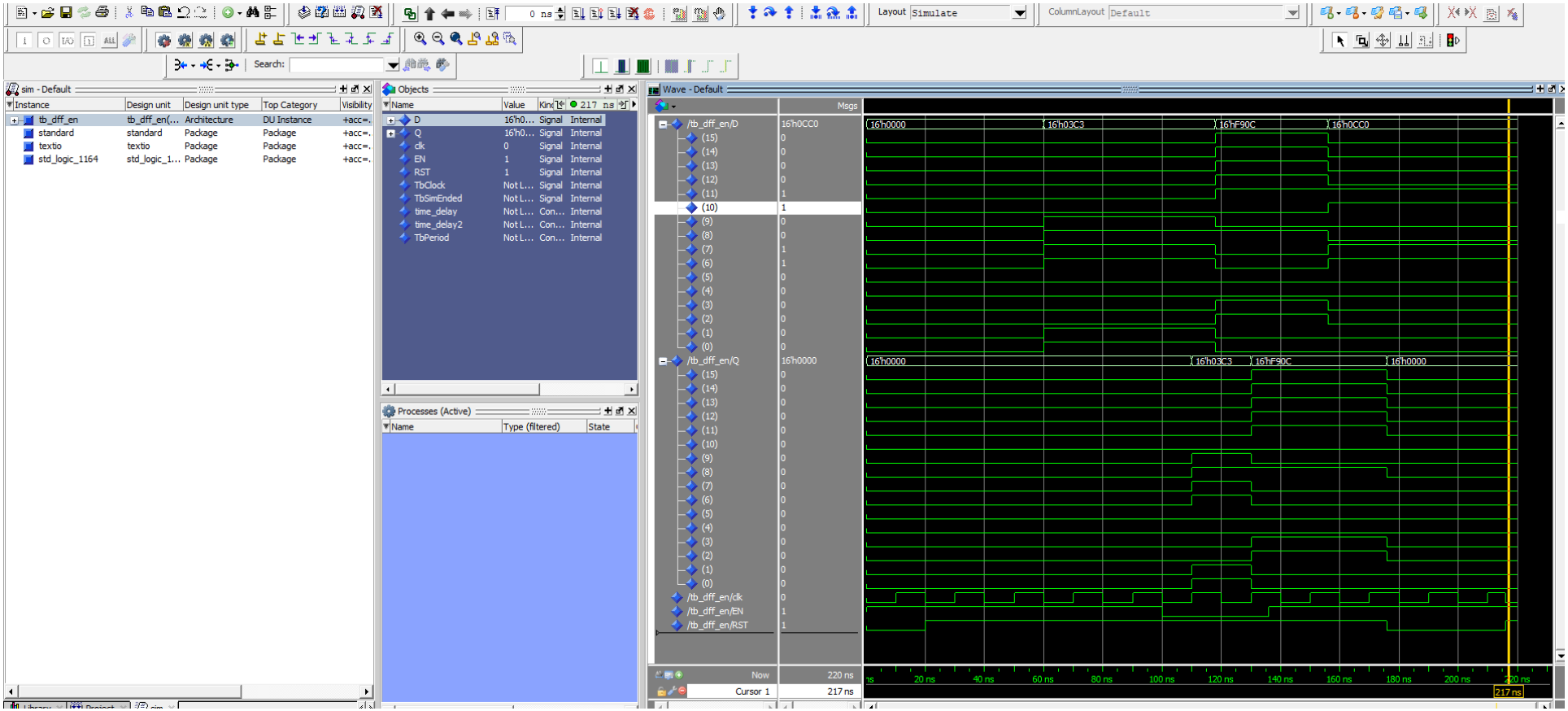

Synchronizer Simulation: